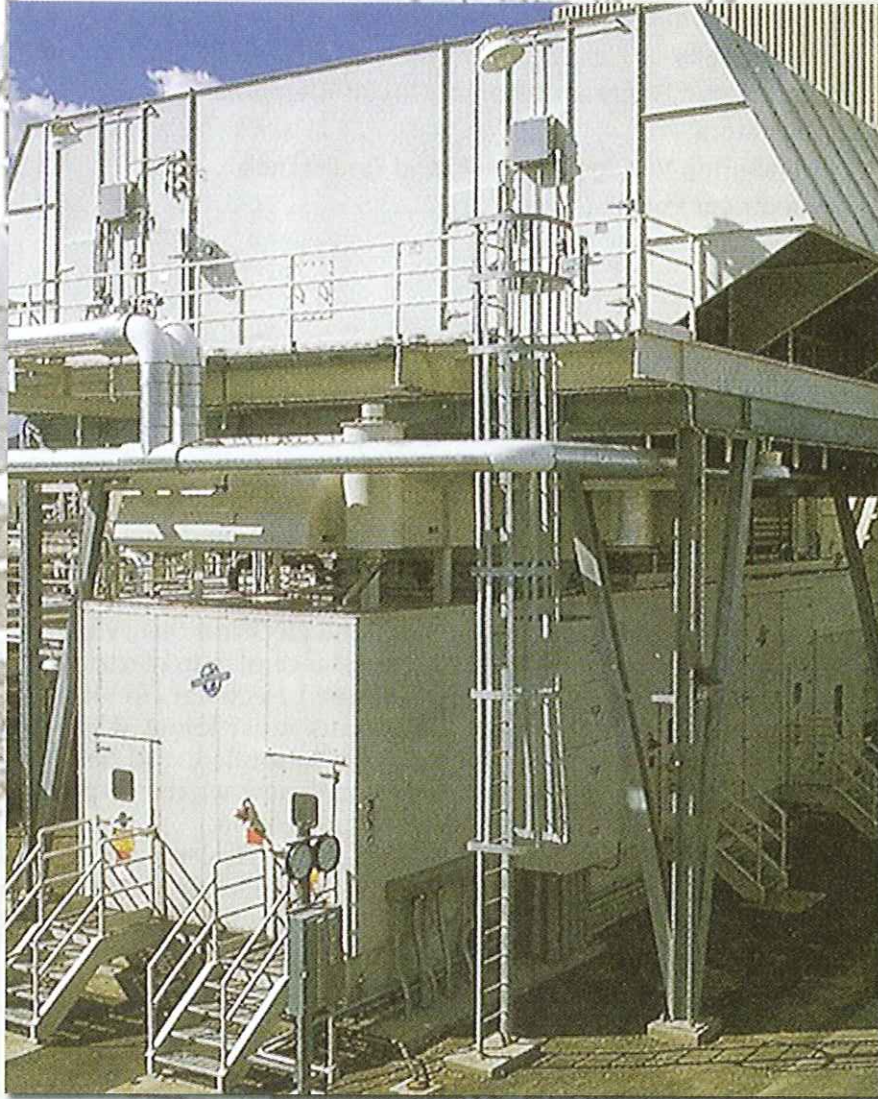


Electrical Theory One

26104-05



Goal Line Cogeneration Power Project

Goal Line is a cogeneration power plant in Escondido, California. A cogeneration power plant produces electricity and steam simultaneously. The combustion turbine at Goal Line burns natural gas and has a capacity of 50 megawatts. Exhaust from the combustion turbine is used to produce steam, and compressors use the steam from Goal Line to produce ice at a local ice-skating arena.


26104-05

Electrical Theory One

Topics to be presented in this module include:

1.0.0	Introduction to Electrical Theory	4.2
2.0.0	Conductors and Insulators	4.2
3.0.0	Electric Charge and Current	4.5
4.0.0	Resistance	4.6
5.0.0	Schematic Representation of Circuit Elements	4.9
6.0.0	Resistors	4.9
7.0.0	Measuring Voltage, Current, and Resistance	4.13
8.0.0	Electrical Power	4.15

Overview

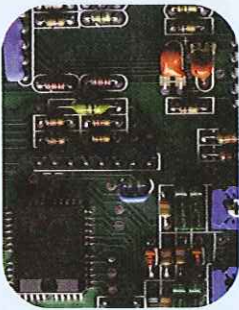

The foundation for successful and safe electrical installations and troubleshooting is a sound understanding of electrical theory. Electrical theory involves the study of atoms, their reactions, and their involvement in electrical circuits. Electricians must understand electrical theory to fully understand the roles that voltage, current, and resistance play in electrical systems.

The primary action in any designed electrical circuit or system is the controlled flow of electrons. Electricians must know what electrons are, what makes them flow, how their flow is controlled, and how this flow is used to perform work. In addition, they must know what to expect if an unintentional or catastrophic flow of electrons should occur.

Having a solid understanding of electrical theory enables electricians to complete quality installations and troubleshoot a circuit or electrical system quickly and efficiently. These skills are fundamental for a successful career as an electrician.

Objectives

When you have completed this module, you will be able to do the following:

1. Recognize what atoms are and how they are constructed.
2. Define voltage and identify the ways in which it can be produced.
3. Explain the difference between conductors and insulators.
4. Define the units of measurement that are used to measure the properties of electricity.
5. Explain how voltage, current, and resistance are related to each other.
6. Using the formula for Ohm's law, calculate an unknown value.
7. Explain the different types of meters used to measure voltage, current, and resistance.
8. Using the power formula, calculate the amount of power used by a circuit.

Trade Terms

Ammeter	Nucleus
Ampere (A)	Ohm (Ω)
Atom	Ohmmeter
Battery	Ohm's law
Circuit	Power
Conductor	Protons
Coulomb	Resistance
Current	Resistor
Electron	Schematic
Insulator	Series circuit
Joule (J)	Valence shell
Kilo	Volt (V)
Matter	Voltage
Mega	Voltage drop
Micro	Voltmeter
Neutrons	Watt (W)


Required Trainee Materials

1. Paper and pencil
2. Appropriate personal protective equipment

Prerequisites

Before you begin this module, it is recommended that you successfully complete *Core Curriculum* and *Electrical Level One*, Modules 26101-05 through 26103-05.

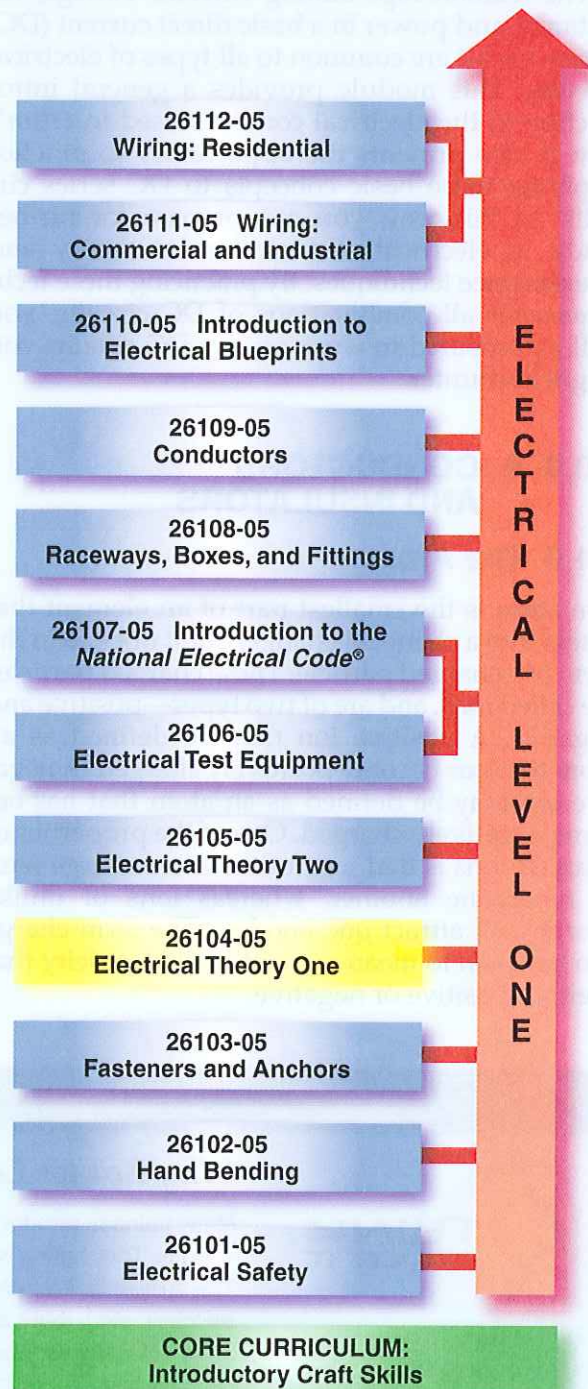This course map shows all of the modules in *Electrical Level One*. The suggested training order begins at the bottom and proceeds up. Skill levels increase as you advance on the course map. The local Training Program Sponsor may adjust the training order.



104CMAPEPS

1.0.0 ♦ INTRODUCTION TO ELECTRICAL THEORY

As an electrician, you must work with a force that cannot be seen. However, electricity is there on the job, every day of the year. It is necessary that you understand the forces of electricity so that you will be safe on the job. The first step is a basic understanding of the principles of electricity.

The relationships among **current**, **voltage**, **resistance**, and **power** in a basic direct current (DC) **series circuit** are common to all types of electrical **circuits**. This module provides a general introduction to the electrical concepts used in **Ohm's law**. It also presents the opportunity to practice applying these basic concepts to DC series circuits. In this way, you can prepare for further study in electrical and electronics theory and maintenance techniques. By practicing these techniques for all combinations of DC circuits, you will be prepared to work on any DC circuits you might encounter.


2.0.0 ♦ CONDUCTORS AND INSULATORS

2.1.0 The Atom

The **atom** is the smallest part of an element that enters into a chemical change, but it does so in the form of a charged particle. These charged particles are called ions, and are of two types—positive and negative. A positive ion may be defined as an atom that has become positively charged. A negative ion may be defined as an atom that has become negatively charged. One of the properties of charged ions is that ions of the same charge tend to repel one another, whereas ions of unlike charge will attract one another. The term charge can be taken to mean a quantity of electricity that is either positive or negative.

The structure of an atom is best explained by a detailed analysis of the simplest of all atoms, that of the element hydrogen. The hydrogen atom in *Figure 1* is composed of a **nucleus** containing one **proton** and a single orbiting **electron**. As the electron revolves around the nucleus, it is held in this orbit by two counteracting forces. One of these forces is called centrifugal force, which is the force that tends to cause the electron to fly outward as it travels around its circular orbit. The second force acting on the electron is electrostatic force. This force tends to pull the electron in toward the nucleus and is provided by the mutual attraction between the positive nucleus and the negative electron. At some given radius, the two forces will balance each other, providing a stable path for the electron.

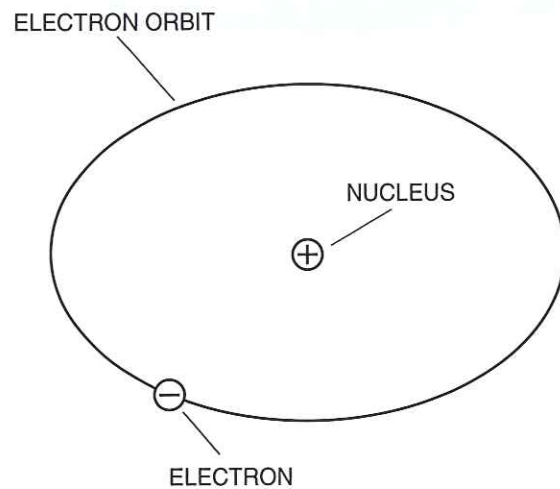- A proton (+) repels another proton (+).
- An electron (-) repels another electron (-).
- A proton (+) attracts an electron (-).



104F01.EPS

Figure 1 ♦ Hydrogen atom.



Why Bother Learning Theory?

Many trainees wonder why they need to bother learning the theory behind how things operate. They figure, why should I learn how it works as long as I know how to install it? The answer is, if you only know how to install something (e.g., run wire, connect switches, etc.), that's all you are ever going to be able to do. For example, if you don't know how your car operates, how can you troubleshoot it? The answer is, you can't. You can only keep changing out the parts until you finally hit on what is causing the problem. (How many times have you seen people do this?) Remember, unless you understand not only how things work but why they work, you'll only be a parts changer. With theory behind you, there is no limit to what you can do.

Basically, an atom contains three types of subatomic particles that are of interest in electricity: electrons, protons, and **neutrons**.

The protons and neutrons are located in the center, or nucleus, of the atom, and the electrons travel about the nucleus in orbits.

Because protons are relatively heavy, the repulsive force they exert on one another in the nucleus of an atom has little effect.

The attracting and repelling forces on charged materials occur because of the electrostatic lines of force that exist around the charged materials. In a negatively charged object, the lines of force of the excess electrons add to produce an electrostatic field that has lines of force coming into the object from all directions. In a positively charged object, the lines of force of the excess protons add to produce an electrostatic field that has lines of force going out of the object in all directions. The electrostatic fields either aid or oppose each other to attract or repel.

2.1.1 The Nucleus

The nucleus is the central part of the atom. It is made up of heavy particles called protons and

neutrons. The proton is a charged particle containing the smallest known unit of positive electricity. The neutron has no electrical charge. The number of protons in the nucleus determines how the atom of one element differs from the atom of another element.

Although a neutron is actually a particle by itself, it is generally thought of as an electron and proton combined and is electrically neutral. Since neutrons are electrically neutral, they are not considered important to the electrical nature of atoms.



2.1.2 Electrical Charges

The negative charge of an electron is equal but opposite to the positive charge of a proton. The charges of an electron and a proton are called electrostatic charges. The lines of force associated with each particle produce electrostatic fields. Because of the way these fields act together, charged particles can attract or repel one another. The Law of Electrical Charges states that particles with like charges repel each other and those with unlike charges attract each other. This is shown in *Figure 2*.

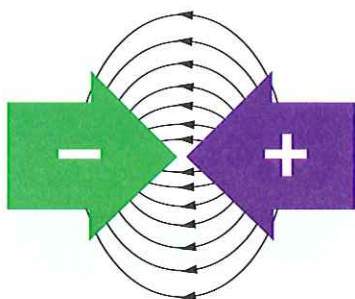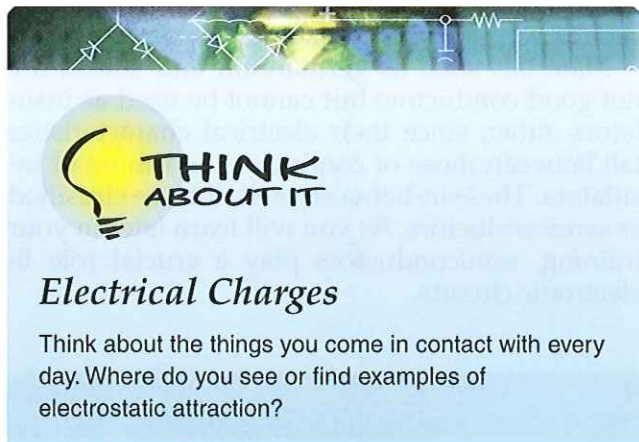
2.2.0 Conductors and Insulators

The difference between atoms, with respect to chemical activity and stability, depends on the number and position of the electrons included within the atom. In general, the electrons reside in groups of orbits called shells. The shells are arranged in steps that correspond to fixed energy levels.

The number of electrons in the outermost shell determines the valence of an atom. For this reason, the outer shell of an atom is called the **valence shell**, and the electrons contained in this shell are called valence electrons (*Figure 3*). The valence of an atom determines its ability to gain or lose an electron, which in turn determines the chemical and electrical properties of the atom. An




UNLIKE CHARGES ATTRACT

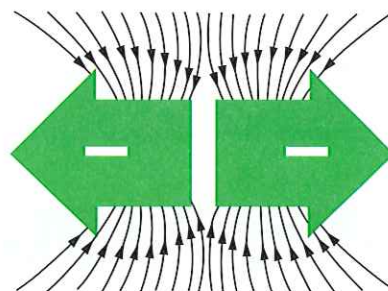

LIKE CHARGES REPEL

104F02.EPS

Figure 2 ♦ Law of electrical charges.

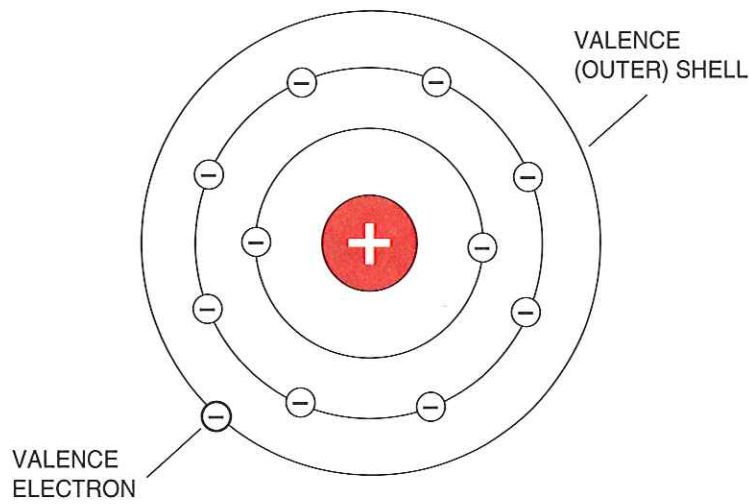

104F03.EPS

Figure 3 ♦ Valence shell and electrons.

atom that is lacking only one or two electrons from its outer shell will easily gain electrons to complete its shell, but a large amount of energy is required to free any of its electrons. An atom having a relatively small number of electrons in its outer shell in comparison to the number of electrons required to fill the shell will easily lose these valence electrons.

It is the valence electrons that we are most concerned with in electricity. These are the electrons that are easiest to break loose from their parent atom. Normally, a **conductor** has three or less valence electrons, an **insulator** has five or more valence electrons, and semiconductors usually have four valence electrons.

All the elements of which **matter** is made may be placed into one of three categories: conductors, insulators, and semiconductors.

Conductors, for example, are elements such as copper and silver that will conduct a flow of electricity very readily. Because of their good conducting abilities, they are formed into wire and used whenever it is desired to transfer electrical energy from one point to another.

Insulators, on the other hand, do not conduct electricity to any great degree and are used when it is desirable to prevent the flow of electricity. Compounds such as porcelain and plastic are good insulators.

Materials such as germanium and silicon are not good conductors but cannot be used as insulators either, since their electrical characteristics fall between those of conductors and those of insulators. These in-between materials are classified as semiconductors. As you will learn later in your training, semiconductors play a crucial role in electronic circuits.



Conductors



Why do some substances conduct? What happens inside a conductor? What makes a good conductor?



Insulating Materials Become Conductive When Wet



While pure (distilled) water is an insulator, even trace levels of minerals make it into a conductor.

3.0.0 ♦ ELECTRIC CHARGE AND CURRENT

An electric charge has the ability to do the work of moving another charge by attraction or repulsion. The ability of a charge to do work is called its potential. When one charge is different from another, there must be a difference in potential between them. The sum of the difference of potential of all the charges in the electrostatic field is referred to as electromotive force (emf) or voltage. Voltage is frequently represented by the letter *E*.

Electric charge is measured in **coulombs**. An electron has 1.6×10^{-19} coulombs of charge. Therefore, it takes 6.25×10^{18} electrons to make up one coulomb of charge, as shown below.

$$\frac{1}{1.6 \times 10^{-19}} = 6.25 \times 10^{18} \text{ electrons}$$

If two particles, one having charge Q_1 and the other charge Q_2 , are a distance (*d*) apart, then the force between them is given by Coulomb's law, which states that the force is directly proportional to the product of the two charges and inversely proportional to the square of the distance between them:

$$\text{Force} = \frac{k \times Q_1 \times Q_2}{d^2}$$

If Q_1 and Q_2 are both positive or both negative, then the force is positive; it is repulsive. If Q_1 and Q_2 are of opposite charges, then the force is negative; it is attractive. The letter *k* equals a constant with a value of 10^9 .

3.1.0 Current Flow

The movement of the flow of electrons is called current. To produce current, the electrons are moved by a potential difference. Current is represented by the letter *I*. The basic unit in which current is measured is the **ampere**, also called the

amp. The symbol for the ampere is *A*. One ampere of current is defined as the movement of one coulomb past any point of a conductor during one second of time. One coulomb is equal to 6.25×10^{18} electrons; therefore, one ampere is equal to 6.25×10^{18} electrons moving past any point of a conductor during one second of time.

The definition of current can be expressed as an equation:

$$I = \frac{Q}{T}$$

Where:

- I* = current (amperes)
- Q* = charge (coulombs)
- T* = time (seconds)

Charge differs from current in that *Q* is an accumulation of charge, while *I* measures the intensity of moving charges.

In a conductor, such as copper wire, the free electrons are charges that can be forced to move with relative ease by a potential difference. If a potential difference is connected across two ends of a copper wire, as shown in *Figure 4*, the applied voltage

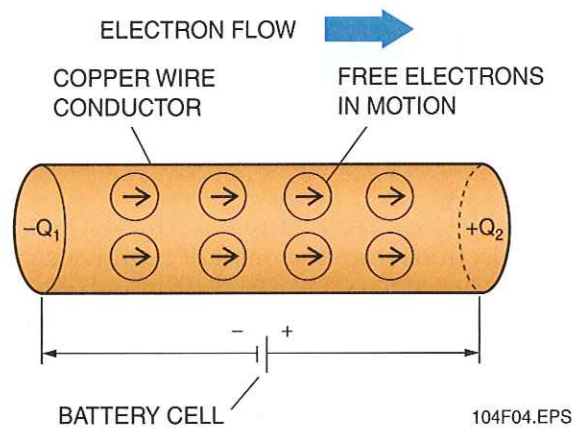



Figure 4 ♦ Potential difference causing electric current.



Units of Electricity and Volta

A disagreement with a fellow scientist over the twitching of a frog's leg eventually led 18th-century physicist Alessandro Volta to theorize that when certain objects and chemicals come into contact with each other, they produce an electric current. Believing that electricity came from contact between metals only, Volta coined the term metallic electricity. To demonstrate his theory, Volta placed two discs, one of silver and the other of zinc, into a weak acidic solution. When he linked the discs together with wire, electricity flowed through the wire. Thus, Volta introduced the world to the battery, also known as the Voltaic pile. Now Volta needed a term to measure the strength of the electric push or the flowing charge; the volt is that measure.



Law of Electrical Force and de Coulomb

In the 18th century, a French physicist named Charles de Coulomb was concerned with how electric charges behaved. He watched the repelling forces electric charges exerted by measuring the twist in a wire. An object's weight acted as a turning force to twist the wire, and the amount of twist was proportional to the object's weight. After many experiments with opposing forces, de Coulomb proposed the Inverse Square Law, later known as the *Law of Electrical Force*.



The Magic of Electricity

The flow of electrons occurs at close to the speed of light, about 186,000 miles per second. How long does it take the light from the end of a flashlight to reach the floor? If you ran a light circuit from Maine to California and flipped the switch, how long would it take for the light to come on?



Current Flow

Why do you need two wires to use electrical devices? Why can't current simply move to a lamp and be released as light energy?

forces the free electrons to move. This current is a flow of electrons from the point of negative charge (–) at one end of the wire, moving through the wire to the positive charge (+) at the other end. The direction of the electron flow is from the negative side of the battery, through the wire, and back to the positive side of the battery. The direction of current flow is therefore from a point of negative potential to a point of positive potential.

3.2.0 Voltage

The force that causes electrons to move is called voltage, potential difference, or electromotive force (emf). One **volt (V)** is the potential difference between two points for which one coulomb of electricity will do one **joule (J)** of work. A **battery** is one of several means of creating voltage. It chemically creates a large reserve of free electrons at the negative (–) terminal. The positive (+) terminal has electrons chemically removed and will therefore accept them if an external path is provided from the negative (–) terminal. When a battery is no longer able to chemically deposit

electrons at the negative (–) terminal, it is said to be dead, or in need of recharging. Batteries are normally rated in volts. Large batteries are also rated in ampere-hours, where one ampere-hour is a current of one amp supplied for one hour.

4.0.0 ♦ RESISTANCE

Resistance is directly related to the ability of a material to conduct electricity. Conductors have very low resistance; insulators have very high resistance.

4.1.0 Characteristics of Resistance

Resistance can be defined as the opposition to current flow. To add resistance to a circuit, electrical components called **resistors** are used. A resistor is a device whose resistance to current flow is a known, specified value. Resistance is measured in ohms and is represented by the symbol R in equations. One **ohm** is defined as the amount of resistance that will limit the current in a conductor to one ampere when the voltage applied to the conductor is one volt. The symbol for an ohm is Ω .



Voltage

Why is voltage called electrical potential? Why are we interested in potential charges—why not simply measure the actual flow of current? Can there be very high potential and no current, or a very small current? What happens when lightning strikes in terms of electrical potential?



Joule's Law

While other scientists of the 19th century were experimenting with batteries, cells, and circuits, James Joule was theorizing about the relationship between heat and energy. He discovered, contrary to popular belief, that work did not just move heat from one place to another; work, in fact, generated heat. Furthermore, he demonstrated that over time, a relationship existed between the temperature of water and electric current. These ideas formed the basis for the concept of energy. In his honor, the modern unit of energy was named the joule.



The Visual Language of Electricity

Learning to read circuit diagrams is like learning to read a book—first you learn to read the letters, then you learn to read the words, and before you know it, you are reading without paying attention to the individual letters anymore. Circuits are the same way—you will struggle at first with the individual pieces, but before you know it, you will be reading a circuit without even thinking about it. Studying the table below will help you to understand the fundamental language of electricity.

What's Measured	Unit of Measurement	Symbol	Ohm's Law Symbol
Amount of current	Amp	A	I
Electrical power	Watt	W	P
Force of current	Volt	V	E
Resistance to current	Ohm	Ω	R

The resistance of a wire is proportional to the length of the wire, inversely proportional to the cross-sectional area of the wire, and dependent upon the kind of material of which the wire is made. The relationship for finding the resistance of a wire is:

$$R = \rho \frac{L}{A}$$

Where:

R = resistance (ohms)

L = length of wire (feet)

A = area of wire (circular mils, CM, or cm^2)

ρ = specific resistance (ohm-CM/ft. or microhm-CM)

A mil equals 0.001 inch; a circular mil is the cross-sectional area of a wire one mil in diameter.

The specific resistance is a constant that depends on the material of which the wire is made. *Table 1* shows the properties of various wire conductors.

Table 1 shows that at 75°F, a one-mil diameter, pure annealed copper wire that is one foot long has a resistance of 10.351 ohms; while a one-mil diameter, one-foot-long aluminum wire has a resistance of 16.758 ohms. Temperature is important in determining the resistance of a wire. The hotter a wire, the greater its resistance.

Table 1 Conductor Properties

Metal	Specific Resistance (Resistance of 1 CM/ft. in ohms)	
	32°F or 0°C	75°F or 23.8°C
Silver, pure annealed	8.831	9.674
Copper, pure annealed	9.390	10.351
Copper, annealed	9.590	10.505
Copper, hard-drawn	9.810	10.745
Gold	13.216	14.404
Aluminum	15.219	16.758
Zinc	34.595	37.957
Iron	54.529	62.643

4.2.0 Ohm's Law

Ohm's law defines the relationship between current, voltage, and resistance. There are three ways to express Ohm's law mathematically.

- The current in a circuit is equal to the voltage applied to the circuit divided by the resistance of the circuit:

$$I = \frac{E}{R}$$

- The resistance of a circuit is equal to the voltage applied to the circuit divided by the current in the circuit:

$$R = \frac{E}{I}$$

- The applied voltage to a circuit is equal to the product of the current and the resistance of the circuit:

$$E = I \times R = IR$$

Where:

- I = current (amperes)
- R = resistance (ohms)
- E = voltage or emf (volts)

If any two of the quantities E, I, or R are known, the third can be calculated.

The Ohm's law equations can be memorized and practiced effectively by using an Ohm's law circle, as shown in Figure 5. To find the equation for E, I, or R when two quantities are known, cover the unknown third quantity. The other two quantities in the circle will indicate how the covered quantity may be found.

Example 1:

Find I when E = 120V and R = 30Ω.

$$I = \frac{E}{R}$$

$$I = \frac{120V}{30\Omega}$$

$$I = 4A$$

This formula shows that in a DC circuit, current (I) is directly proportional to voltage (E) and inversely proportional to resistance (R).

Example 2:

Find R when E = 240V and I = 20A.

$$R = \frac{E}{I}$$

$$R = \frac{240V}{20A}$$

$$R = 12\Omega$$


Example 3:

Find E when I = 15A and R = 8Ω.

$$E = I \times R$$

$$E = 15A \times 8\Omega$$

$$E = 120V$$

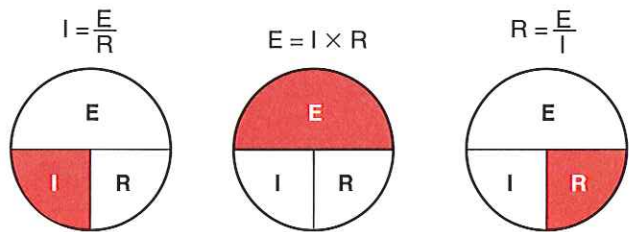

	LETTER SYMBOL	UNIT OF MEASUREMENT
CURRENT	I	AMPERES (A)
RESISTANCE	R	OHMS (Ω)
VOLTAGE	E	VOLTS (V)

104F05.EPS

Figure 5 ♦ Ohm's law circle.



Voltage Matters

Standard household voltage is different the world over, from 100V in Japan to 600V in Bombay, India. Many countries have no standard voltage; for example, France varies from 110V to 360V. If you were to plug a 120V hair dryer into England's 240V, you would burn out the dryer. Use basic electric theory to explain exactly what would happen to destroy the hair dryer.



Using Ohm's Law

Study the resistance values in *Table 1*. Assuming the same length and area of wire, approximately how much will the current decrease from copper annealed wire to aluminum wire to iron wire?

5.0.0 ◆ SCHEMATIC REPRESENTATION OF CIRCUIT ELEMENTS

A simple electric circuit is shown in both pictorial and schematic forms in *Figure 6*. The schematic diagram is a shorthand way to draw an electric circuit, and circuits are usually represented in this way. In addition to the connecting wire, three components are shown symbolically: the battery, the switch, and the lamp. Note the positive (+) and negative (-) markings in both the pictorial and schematic representations of the battery. The schematic components represent the pictorial components in a simplified manner. A schematic diagram is one that shows, by means of graphic symbols, the electrical connections and functions of the different parts of a circuit.

The standard graphic symbols for commonly used electrical and electronic components are shown in *Figure 7*.

6.0.0 ◆ RESISTORS

The function of a resistor is to offer a particular resistance to current flow. For a given current and known resistance, the change in voltage across the component, or **voltage drop**, can be predicted using Ohm's law. Voltage drop refers to a specific amount of voltage used, or developed, by that component. An example is a very basic circuit of a 10V battery and a single resistor in a series circuit. The voltage drop across that resistor is 10V because it is the only component in the circuit and all voltage must be dropped across that resistor. Similarly, for a given applied voltage, the current that flows may be predetermined by selection of the resistor value. The required power dissipation largely dictates the construction and physical size of a resistor.

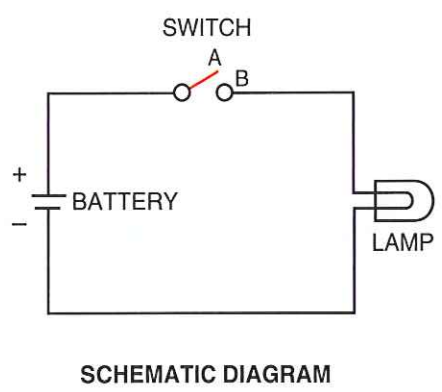
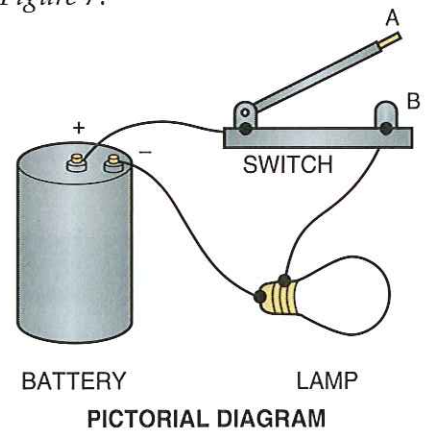


Figure 6 ◆ Simple electrical symbols.

104F06.EPS

Ammeter		Motor (DC)	
Battery		Resistor (fixed)	
Capacitor (fixed)		Resistor (variable)	
Capacitor (variable)		Rheostat	
Circuit breaker		Switch	
Crystal		Semiconductor diode	
Fuse		Transformer (general)	
Generator (AC)		Transformer (iron-core)	
Generator (DC)		Transistor (NPN)	
Ground		Transistor (PNP)	
Inductor (air-core)		Voltmeter	
Inductor (iron-core)		Wattmeter	
Inductor (tapped)		Wires (connected)	
Lamp		Wires (unconnected)	
Motor (AC)		Zener diode	


104F07.EPS

Figure 7 ♦ Standard schematic symbols.

The two most common types of electronic resistors are wire-wound and carbon composition construction. A typical wire-wound resistor consists of a length of nickel wire wound on a ceramic tube and covered with porcelain. Low-resistance connecting wires are provided, and the resistance value is usually printed on the side of the component. *Figure 8* illustrates the construction of typical resistors. Carbon composition resistors are constructed by molding mixtures of powdered carbon and insulating materials into a cylindrical shape. An outer sheath of insulating material af-


fords mechanical and electrical protection, and copper connecting wires are provided at each end. Carbon composition resistors are smaller and less expensive than the wire-wound type. However, the wire-wound type is the more rugged of the two and is able to survive much larger power dissipations than the carbon composition type.


Most resistors have standard fixed values, so they can be termed fixed resistors. Variable resistors, also known as adjustable resistors, are used a great deal in electronics. Two common symbols for a variable resistor are shown in *Figure 9*.




Drawing a Schematic

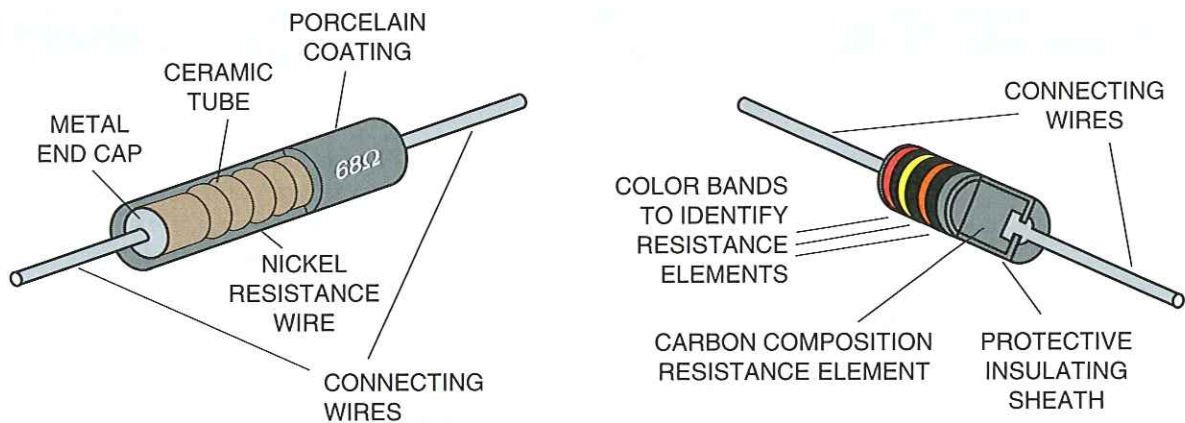Draw a schematic diagram showing a voltage source, switch, motor, and fuse.






104F08A.EPS

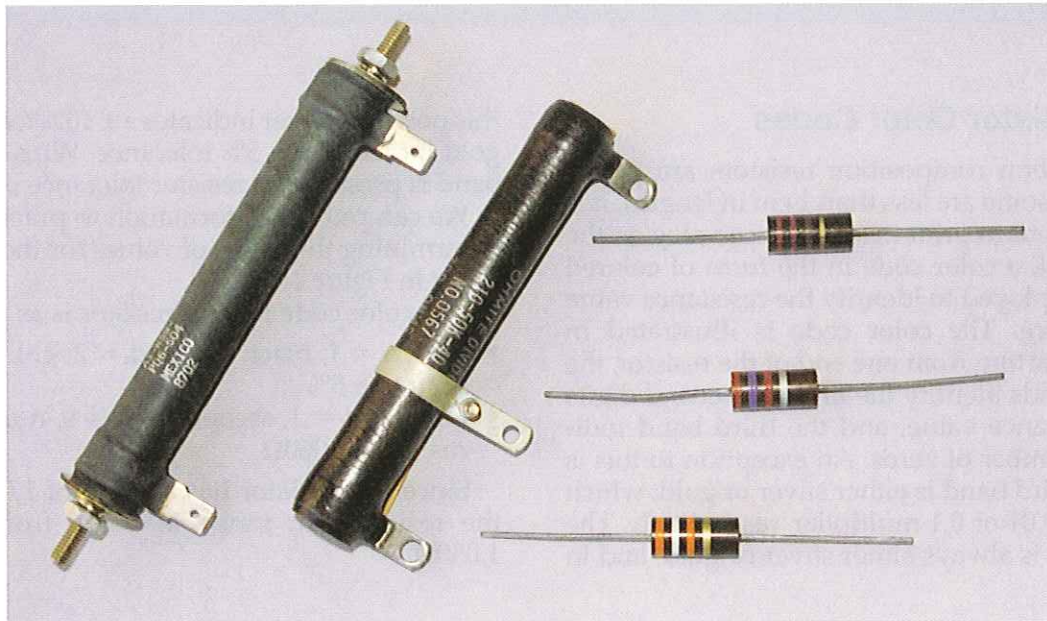

104F08B.EPS

Figure 8 ♦ Common resistors.

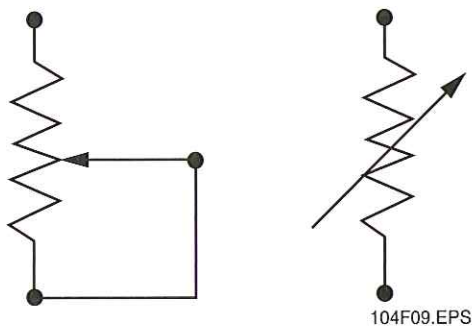

104F09.EPS

Figure 9 ♦ Symbols used for variable resistors.

A variable resistor consists of a coil of closely wound insulated resistance wire formed into a partial circle. The coil has a low-resistance terminal at each end, and a third terminal is connected to a movable contact with a shaft adjustment facility. The movable contact can be set to any point on a connecting track that extends over one (uninsulated) edge of the coil.

Using the adjustable contact, the resistance from either end terminal to the center terminal may be adjusted from zero to the maximum coil resistance.

Another type of variable resistor is known as a decade resistance box. This is a laboratory component that contains precise values of switched series-connected resistors.



Using Your Intuition

Learning the meanings of various electrical symbols may seem overwhelming, but if you take a moment to study *Figure 7*, you will see that most of them are intuitive—that is, they are shaped (in a symbolic way) to represent the actual object. For example, the battery shows + and –, just like an actual battery. The motor has two arms that suggest a spinning rotor. The transformer shows two coils. The resistor has a jagged edge to suggest pulling or resistance. Connected wires have a black dot that reminds you of solder. Unconnected wires simply cross. The fuse stretches out in both directions as though to provide extra slack in the line. The circuit breaker shows a line with a break in it. The capacitor shows a gap. The variable resistor has an arrow like a swinging compass needle. As you learn to read schematics, take the time to make mental connections between the symbol and the object it represents.

6.1.0 Resistor Color Codes

Because carbon composition resistors are physically small (some are less than 1 cm in length), it is not convenient to print the resistance value on the side. Instead, a color code in the form of colored bands is employed to identify the resistance value and tolerance. The color code is illustrated in *Figure 10*. Starting from one end of the resistor, the first two bands identify the first and second digits of the resistance value, and the third band indicates the number of zeros. An exception to this is when the third band is either silver or gold, which indicates a 0.01 or 0.1 multiplier, respectively. The fourth band is always either silver or gold, and in


this position, silver indicates a $\pm 10\%$ tolerance and gold indicates a $\pm 5\%$ tolerance. Where no fourth band is present, the resistor tolerance is $\pm 20\%$.

We can put this information to practical use by determining the range of values for the carbon resistor in *Figure 11*.

The color code for this resistor is as follows:


- Brown = 1, black = 0, red = 2, gold = a tolerance of $\pm 5\%$
- First digit = 1, second digit = 0, number of zeros (2) = 1,000 Ω

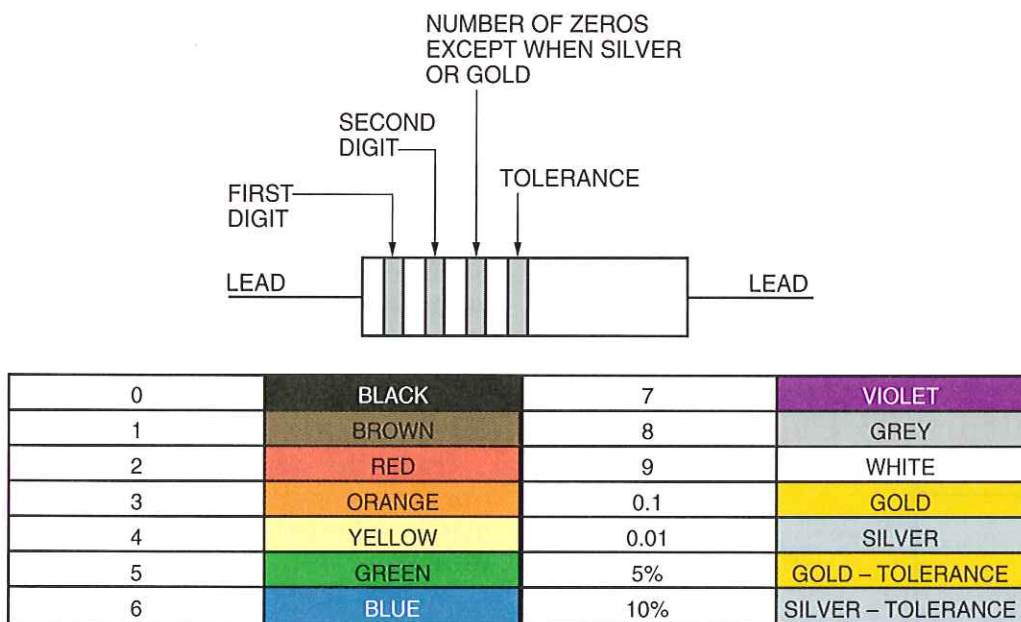Since this resistor has a value of 1,000 $\Omega \pm 5\%$, the resistor can range in value from 950 Ω to 1,050 Ω .



104F10.EPS

Figure 10 ♦ Resistor color codes.

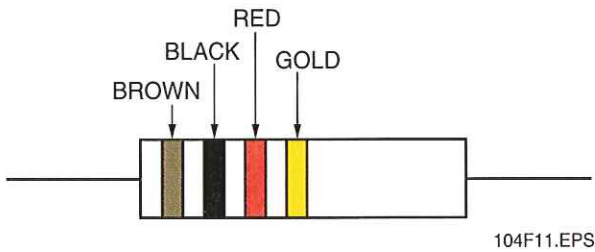

104F11.EPS

Figure 11 ♦ Sample color codes on a fixed resistor.

7.0.0 ♦ MEASURING VOLTAGE, CURRENT, AND RESISTANCE

Working with electricity requires making accurate measurements. This section will discuss the basic meters used to measure voltage, current, and resistance: the **voltmeter**, **ammeter**, and **ohmmeter**.



WARNING!

Only qualified individuals may use these meters. Consult your company's safety policy for applicable rules.

7.1.0 Basic Meter Operation

When troubleshooting or testing equipment, you will need various meters to check for proper circuit voltages, currents, and resistances and to determine if the wiring is defective. Meters are used in repairing, maintaining, and troubleshooting electrical circuits and equipment. The best and most expensive measuring instrument is of no use to you unless you know what you are measuring and what each reading indicates. Remember that the purpose of a meter is to measure quantities existing within a circuit. For this reason, when the meter is connected to a circuit, it must not change the condition of the circuit.

The three basic electrical quantities discussed in this section are current, voltage, and resistance.


Actually, it is really current that causes the meter to respond even when voltage or resistance is being measured. In a basic meter, the measurement of current can be calibrated to indicate almost any electrical quantity based on the principle of Ohm's law. The amount of current that flows through a meter is determined by the voltage applied to the meter and the resistance of the meter, as stated by $I = E/R$.

For a given meter resistance, different values of applied voltage will cause specific values of current to flow. Although the meter actually measures current, the meter scale can be calibrated in units of voltage. Similarly, for a given applied voltage, different values of resistance will cause specific values of current to flow; therefore, the meter scale can also be calibrated in units of resistance rather than current. The same holds true for power, since power is proportional to current, as stated by $P = EI$. It is on this principle that the meter was developed and its construction allows for the measurement of various parameters by actually measuring current.

You must understand the purpose and function of each individual piece of test equipment and any limitations associated with it. It is also extremely important that you understand how to safely use each piece of equipment. If you understand the capabilities of the test equipment, you can better use the equipment, better understand the indications on the equipment, and know what substitute or backup meters can be used.

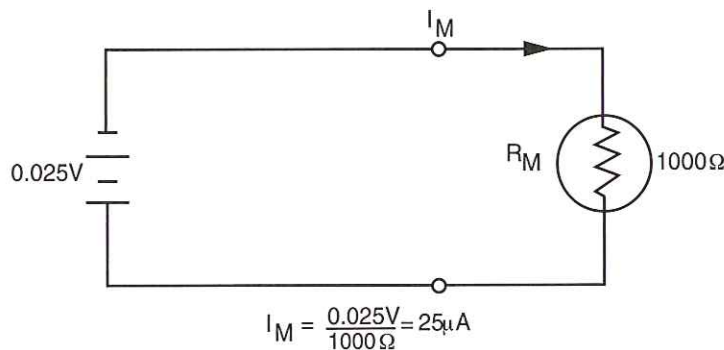7.2.0 Voltmeter

A simple voltmeter consists of the meter movement in series with the internal resistance of the voltmeter itself. For example, a meter with a 50-microamp (μA) meter movement and a $1,000\Omega$ internal resistance can be used to directly measure voltages up to 0.05V , as shown in Figure 12. (The prefix **micro** means one-millionth.) When the meter is placed across the voltage source, a current



104F12.EPS

Figure 12 ♦ Simple voltmeter.

determined by the internal resistance of the meter flows through the meter movement. A voltmeter's internal resistance is typically high to minimize meter loading effects on the source.

To measure larger voltages, a multiplier resistor is used. This increased series resistance limits the current that can flow through the meter movement, thus extending the range of the meter.

To avoid damage to the meter movement, the following precautions should be observed when using a voltmeter:


- Always set the full-scale voltage of the meter to be larger than the expected voltage to be measured.
- Always ensure that the internal resistance of the voltmeter is much greater than the resistance of the component to be measured. This means that the current it takes to drive the voltmeter (about 50 microamps) should be a negligible fraction of the current flowing through the circuit element being measured.
- If you are unsure of the level of the voltage to be measured, take a reading at the highest range of the voltmeter and progressively (step-by-step) lower the range until the reading is obtained.

In most commercial voltmeters, the internal resistance is expressed by the ohms-per-volt rating of the meter. A typical meter has a rating of 20,000 ohms-per-volt with a 50-microamp movement. This quantity tells what the internal resistance of the meter is on any particular full-scale setting. In general, the meter's internal resistance is the ohms-per-volt rating multiplied by the full-scale voltage. The higher the ohms-per-volt rating, the higher the internal resistance of the meter, and the smaller the effect of the meter on the circuit.

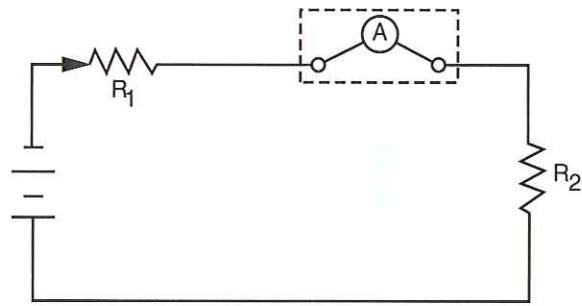7.3.0 Ammeter

A current meter, usually called an ammeter, is used by placing the meter in series with the wire through which the current is flowing. This method of connection is shown in *Figure 13*. Notice how the magnitude of load current will flow through the ammeter. Because of this, an ammeter's internal resistance must be low to minimize the circuit-loading effects as seen by the source. Also, high current magnitudes flowing through an ammeter can damage it. For this reason, ammeter shunts are employed to reduce the ammeter circuit current to a fraction of the current flowing through the load.

To avoid damage to the meter movement, the following precautions should be observed when taking current measurements with an ammeter:




104F13.EPS

Figure 13 ♦ Ammeter connection.

- Always check the polarity of the ammeter. Make certain that the meter is connected to the circuit so that electrons flow into the negative lead and out of the positive lead. It is easy to tell which is the positive lead because it is normally red. The negative lead is usually black.
- Always set the full-scale deflection of the meter to be larger than the expected current. To be safe, set the full-scale current several times larger than the expected current, and then slowly increase the meter sensitivity to the appropriate scale.
- Always connect the ammeter in series with the circuit element through which the current to be measured is flowing. Never connect the ammeter in parallel. When an ammeter is connected across a constant-potential source of appreciable voltage, the low internal resistance of the meter bypasses the circuit resistance. This results in the application of the source voltage directly to the meter terminals. The resulting excess current will burn out the meter coil.

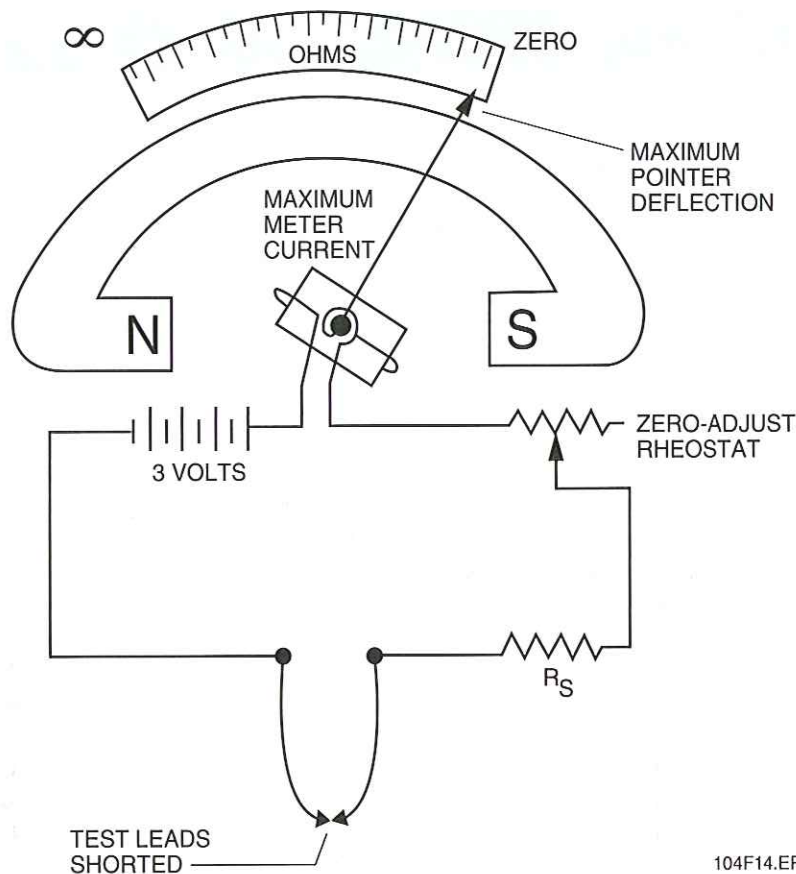
7.4.0 Ohmmeter


An ohmmeter is used to measure resistance and check continuity. The deflection of the pointer of an ohmmeter is controlled by the amount of battery current passing through the coil. Current flow depends on the applied voltage and the circuit resistance. By applying a constant source voltage to the circuit under test, the resultant current flow depends only on circuit resistance. This magnitude of current will create meter movement. By knowing the relationship between current and resistance, an ohmmeter's scale can be calibrated to indicate circuit resistance based on the magnitude of current for a constant source voltage. Refer to *Figure 14*, a simple ohmmeter circuit.



104F14.EPS

Figure 14 ♦ Simple ohmmeter circuit.





Using an Ohmmeter

An ohmmeter has its own battery to test the resistance or continuity of a circuit. Therefore, the circuit must be de-energized because the ohmmeter is calibrated for its own power source.

8.0.0 ♦ ELECTRICAL POWER

Power is defined as the rate of doing work. This is equivalent to the rate at which energy is used or dissipated. Electrons passing through a resistance dissipate energy in the form of heat. In electrical circuits, power is measured in units called **watts (W)**. The power in watts equals the rate of energy conversion. One watt of power equals the work done in one second by one volt of potential difference in moving one coulomb of charge. One coulomb per second is an ampere; therefore, power in watts equals the product of amperes times volts.

The work done in an electrical circuit can be useful work or it can be wasted work. In both

cases, the rate at which the work is done is still measured in power. The turning of an electric motor is useful work. On the other hand, the heating of wires or resistors in a circuit is wasted work, since no useful function is performed by the heat.

The unit of electrical work is the joule. This is the amount of work done by one coulomb flowing through a potential difference of one volt. Thus, if five coulombs flow through a potential difference of one volt, five joules of work are done. The time it takes these coulombs to flow through the potential difference has no bearing on the amount of work done.



Power

We take electrical power for granted, never stopping to think how surprising it is that a flow of submicroscopic electrons can pump thousands of gallons of water or illuminate a skyscraper. Our lives now constantly rely on the ability of the electron to do work. Think about your day up to this moment. How has electrical power shaped your experience?

It is more convenient when working with circuits to think of amperes of current rather than coulombs. As previously discussed, one ampere equals one coulomb passing a point in one second. Using amperes, one joule of work is done in one second when one ampere moves through a potential difference of one volt. This rate of one joule of work in one second is the basic unit of power, and is called a watt. Therefore, a watt is the power used when one ampere of current flows through a potential difference of one volt, as shown in *Figure 15*.

Mechanical power is usually measured in units of horsepower (hp). To convert from horsepower to watts, multiply the number of horsepower by 746. To convert from watts to horsepower, divide the number of watts by 746. Conversions for common units of power are given in *Table 2*.

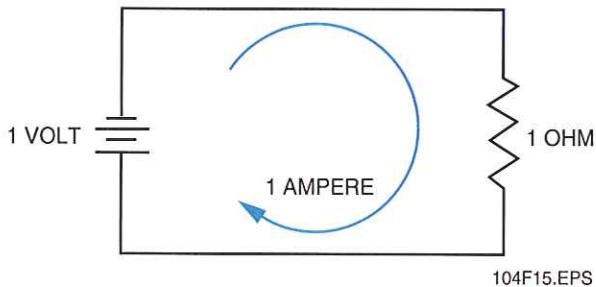


Figure 15 ♦ One watt.

The kilowatt-hour (kWh) is commonly used for large amounts of electrical work or energy. (The prefix **kilo** means one thousand.) The amount is calculated simply as the product of the power in kilowatts multiplied by the time in hours during which the power is used. If a light bulb uses 300W or 0.3kW for 4 hours, the amount of energy is 0.3×4 , which equals 1.2kWh.

Very large amounts of electrical work or energy are measured in megawatts (MW). (The prefix **mega** means one million.)

Electricity usage is figured in kilowatt-hours of energy. The power line voltage is fairly constant at 120V. Suppose the total load current in the main line equals 20A. Then the power in watts from the 120V line is:

$$P = 120V \times 20A$$

$$P = 2,400W \text{ or } 2.4kW$$

If this power is used for five hours, then the energy of work supplied equals:

$$2.4 \times 5 = 12kWh$$

Table 2 Conversion Table

1,000 watts (W) = 1 kilowatt (kW)
1,000,000 watts (W) = 1 megawatt (MW)
1,000 kilowatts (kW) = 1 megawatt (MW)
1 watt (W) = 0.00134 horsepower (hp)
1 horsepower (hp) = 746 watts (W)



Resistors

Which of the following items are resistors?

- Hair dryer
- Incandescent light bulb
- Switch
- Receptacle
- Circuit breaker

8.1.0 Power Equation

When one ampere flows through a difference of two volts, two watts must be used. In other words, the number of watts used is equal to the number of amperes of current times the potential difference. This is expressed in equation form as:

$$P = I \times E \text{ or } P = IE$$

Where:

P = power used in watts

I = current in amperes

E = potential difference in volts

The equation is sometimes called Ohm's law for power, because it is similar to Ohm's law. This equation is used to find the power consumed in a circuit or load when the values of current and voltage are known. The second form of the equation is used to find the voltage when the power and current are known:

$$E = \frac{P}{I}$$

The third form of the equation is used to find the current when the power and voltage are known:

$$I = \frac{P}{E}$$

Using these three equations, the power, voltage, or current in a circuit can be calculated whenever any two of the values are already known.

Example 1:

Calculate the power in a circuit where the source of 100V produces 2A in a 50Ω resistance.

$$P = IE$$

$$P = 2 \times 100$$

$$P = 200W$$

This means the source generates 200W of power while the resistance dissipates 200W in the form of heat.

Example 2:

Calculate the source voltage in a circuit that consumes 1,200W at a current of 5A.

$$E = \frac{P}{I}$$

$$E = \frac{1,200}{5}$$

$$E = 240V$$

Example 3:

Calculate the current in a circuit that consumes 600W with a source voltage of 120V.

$$I = \frac{P}{E}$$

$$I = \frac{600}{120}$$

$$I = 5A$$

Components that use the power dissipated in their resistance are generally rated in terms of power. The power is rated at normal operating voltage, which is usually 120V. For instance, an appliance that draws 5A at 120V would dissipate 600W. The rating for the appliance would then be 600W/120V.

To calculate I or R for components rated in terms of power at a specified voltage, it may be convenient to use the power formula in different forms. There are actually three basic power formulas, but each can be rearranged into two other forms for a total of nine combinations:

$$P = IE$$

$$P = I^2R$$

$$P = \frac{E^2}{R}$$

$$I = \frac{P}{E}$$

$$R = \frac{P}{I^2}$$


$$R = \frac{E^2}{P}$$

$$E = \frac{P}{I}$$

$$I = \sqrt{\frac{P}{R}}$$

$$E = \sqrt{PR}$$

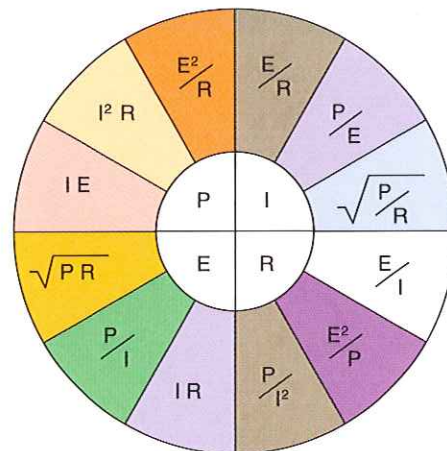Note that all of these formulas are based on Ohm's law ($E = IR$) and the power formula ($P = I \times E$). *Figure 16* shows all of the applicable power, voltage, resistance, and current equations.



104F16.EPS

Figure 16 ♦ Expanded Ohm's law circle.



Measuring Watts

Electricians are less interested in measuring watts than in measuring amperage and resistance. Who would be most interested in power measurements? What is a common example of a device used to measure watts?

8.2.0 Power Rating of Resistors

If too much current flows through a resistor, the heat caused by the current will damage or destroy the resistor. This heat is caused by I^2R heating, which is power loss expressed in watts. Therefore, every resistor is given a wattage, or power rating, to show how much I^2R heating it can take before it burns out. This means that a resistor with a power rating of one watt will burn out if it is used in a circuit where the current causes it to dissipate heat at a rate greater than one watt.

If the power rating of a resistor is known, the maximum current it can carry is found by using an equation derived from $P = I^2R$:

$$P = I^2R \text{ becomes } I^2 = P/R,$$
$$\text{which becomes } I = \sqrt{P/R}$$

Using this equation, find the maximum current that can be carried by a 1Ω resistor with a power rating of 4W:

$$I = \sqrt{P/R} = \sqrt{4/1} = 2 \text{ amperes}$$

If such a resistor conducts more than 2 amperes, it will dissipate more than its rated power and burn out.

Power ratings assigned by resistor manufacturers are usually based on the resistors being mounted in an open location where there is free air circulation, and where the temperature is not higher than 104°F (40°C). Therefore, if a resistor is mounted in a small, crowded, enclosed space, or where the temperature is higher than 104°F , there is a good chance it will burn out even before its power rating is exceeded. Also, some resistors are designed to be attached to a chassis or frame that will carry away the heat.



Putting It All Together

Notice the common electrical devices in the building you're in. What is their wattage rating? How much current do they draw? How would you test their voltage or amperage?

A background image featuring a complex circuit diagram with various components like resistors, capacitors, and diodes. A blue rounded rectangle with a green border is centered at the top, containing the word 'Summary'.

Summary

The relationships among current, voltage, resistance, and power are consistent for all types of DC circuits and can be calculated using Ohm's law

and Ohm's law for power. Understanding and being able to apply these concepts is necessary for effective circuit analysis and troubleshooting.

A blue rounded rectangle with a green border, centered horizontally, containing the word 'Notes'.

Notes


Trade Terms

Ammeter
Ampere (A)
Atom
Battery
Circuit
Conductor
Coulomb
Current

Electron
Insulator
Joule (J)
Kilo
Matter
Mega
Micro
Neutrons

Nucleus
Ohm (Ω)
Ohmmeter
Ohm's law
Power
Protons
Resistance
Resistor

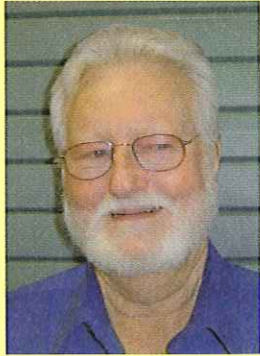Schematic
Series circuit
Valence shell
Volt (V)
Voltage
Voltage drop
Voltmeter
Watt (W)



E. L. Jarrell

Associated Builders and Contractors

Eurlin Layne (E.L.) Jarrell is another prime example of a master electrician giving back to the electrical community by teaching and mentoring.

After serving in the United States Army, E.L. went to work for Cities Services, now known as CITGO. He stayed at CITGO for 38 years, finally retiring in 1995. It was during his employment at CITGO that he first received apprenticeship training in the electrical field.

While at CITGO, E.L. worked as a process unit operator before moving to the electrical department. While there, he worked as a trainee electrician for three years until he became a first-class electrician. A few years later, he was promoted to temporary supervisor, planning and scheduling shut-down maintenance. In 1983, he took and passed the Block Master Electrician test for the City of Lake Charles, Louisiana. In 1997, E.L. became involved with Associated Builders and Contractors (ABC).

E.L. is currently the Electrical Department Head for the ABC Training Center, where he works in the lab, overseeing students doing hands-on electrical work. During his first semester teaching at the ABC

Training Center, it became clear to E.L. that many students simply had no time to study because they worked 10-hour days, drove over 100 miles to work, and had family obligations. In response, E.L. began an in-class study guide. He encouraged students to form study groups, and he gave students time to study in class.

E.L. was an instrumental member of NCCER's Technical Review Committee, which completely rewrote all four levels of NCCER's Electrical Curriculum. In addition, E.L. is currently a member of both NCCER's National Skills Assessment Written Test Committee and the Performance Verification Packet for Industrial Electricians Committee.

E.L. has decided to give back to the electrical community with his expertise and mentoring. Many of E.L.'s students have become his personal friends. He says, "At this point in my life, I just want to continue being the best electrical instructor that I can be and share some of my knowledge and experience with my students and hope that I can make a difference in their lives and careers."

Trade Terms Introduced in This Module

Ammeter: An instrument for measuring electrical current.

Ampere (A): A unit of electrical current. For example, one volt across one ohm of resistance causes a current flow of one ampere.

Atom: The smallest particle to which an element may be divided and still retain the properties of the element.

Battery: A DC voltage source consisting of two or more cells that convert chemical energy into electrical energy.

Circuit: A complete path for current flow.

Conductor: A material that offers very little resistance to current flow.

Coulomb: An electrical charge equal to 6.25×10^{18} electrons or 6,250,000,000,000,000 electrons. A coulomb is the common unit of quantity used for specifying the size of a given charge.

Current: The movement, or flow, of electrons in a circuit. Current (I) is measured in amperes.

Electron: A negatively charged particle that orbits the nucleus of an atom.

Insulator: A material that offers resistance to current flow.

Joule (J): A unit of measurement that represents one newton-meter (Nm), which is a unit of measure for doing work.

Kilo: A prefix used to indicate one thousand; for example, one kilowatt is equal to one thousand watts.

Matter: Any substance that has mass and occupies space.

Mega: A prefix used to indicate one million; for example, one megawatt is equal to one million watts.

Micro: A prefix used to indicate one-millionth; for example, one microwatt is equal to one-millionth of a watt.

Neutrons: Electrically neutral particles (neither positive nor negative) that have the same mass as a proton and are found in the nucleus of an atom.

Nucleus: The center of an atom. It contains the protons and neutrons of the atom.

Ohm (Ω): The basic unit of measurement for resistance.

Ohmmeter: An instrument used for measuring resistance.

Ohm's law: A statement of the relationships among current, voltage, and resistance in an electrical circuit: current (I) equals voltage (E) divided by resistance (R). Generally expressed as a mathematical formula: $I = E/R$.

Power: The rate of doing work or the rate at which energy is used or dissipated. Electrical power is the rate of doing electrical work. Electrical power is measured in watts.

Protons: The smallest positively charged particles of an atom. Protons are contained in the nucleus of an atom.

Resistance: An electrical property that opposes the flow of current through a circuit. Resistance (R) is measured in ohms.

Resistor: Any device in a circuit that resists the flow of electrons.

Schematic: A type of drawing in which symbols are used to represent the components in a system.

Series circuit: A circuit with only one path for current flow.

Valence shell: The outermost ring of electrons that orbit about the nucleus of an atom.

Volt (V): The unit of measurement for voltage (electromotive force). One volt is equivalent to the force required to produce a current of one ampere through a resistance of one ohm.

Voltage: The driving force that makes current flow in a circuit. Voltage (E) is also referred to as electromotive force or potential.

Voltage drop: The change in voltage across a component that is caused by the current flowing through it and the amount of resistance opposing it.

Voltmeter: An instrument for measuring voltage. The resistance of the voltmeter is fixed. When the voltmeter is connected to a circuit, the current passing through the meter will be directly proportional to the voltage at the connection points.

Watt (W): The basic unit of measurement for electrical power.



Additional Resources

This module is intended to present thorough resources for task training. The following reference works are suggested for further study. These are optional materials for continued education rather than for task training.

Electronics Fundamentals: Circuits, Devices, and Applications, Thomas L. Floyd. New York: Prentice Hall.

Principles of Electric Circuits, Thomas L. Floyd. New York: Prentice Hall.

CONTREN® LEARNING SERIES — USER FEEDBACK

The NCCER makes every effort to keep these textbooks up-to-date and free of technical errors. We appreciate your help in this process. If you have an idea for improving this textbook, or if you find an error, a typographical mistake, or an inaccuracy in NCCER's *Contren*® textbooks, please write us, using this form or a photocopy. Be sure to include the exact module number, page number, a detailed description, and the correction, if applicable. Your input will be brought to the attention of the Technical Review Committee. Thank you for your assistance.

Instructors – If you found that additional materials were necessary in order to teach this module effectively, please let us know so that we may include them in the Equipment/Materials list in the Annotated Instructor's Guide.

Write: Product Development
National Center for Construction Education and Research
P.O. Box 141104, Gainesville, FL 32614-1104

Fax: 352-334-0932

E-mail: curriculum@nccer.org

Craft	Module Name	
Copyright Date	Module Number	Page Number(s)
Description		
(Optional) Correction		
(Optional) Your Name and Address		